

第八章

模拟集成电路中的单元电路

8.1 电流源和电流镜

8.2 差动放大级

8.3 集成运放



8.1 电流源和电流镜

一. 镜像电流源

基准电流:

$$I_{REF} = \frac{V_{CC} - V_{BE}}{R}$$


因为: $V_{BE2} = V_{BE1}$

所以: $I_{B2} = I_{B1}$ $I_{C2} = I_{C1}$

$$I_{REF} = I_{C1} + I_{B1} + I_{B2} = I_{C1}(1 + 2/\beta)$$

$$I_{C2} = I_{REF} / (1 + 2/\beta)$$

无论 R_c 的值如何, I_{C2} 的电流值将保持不变。

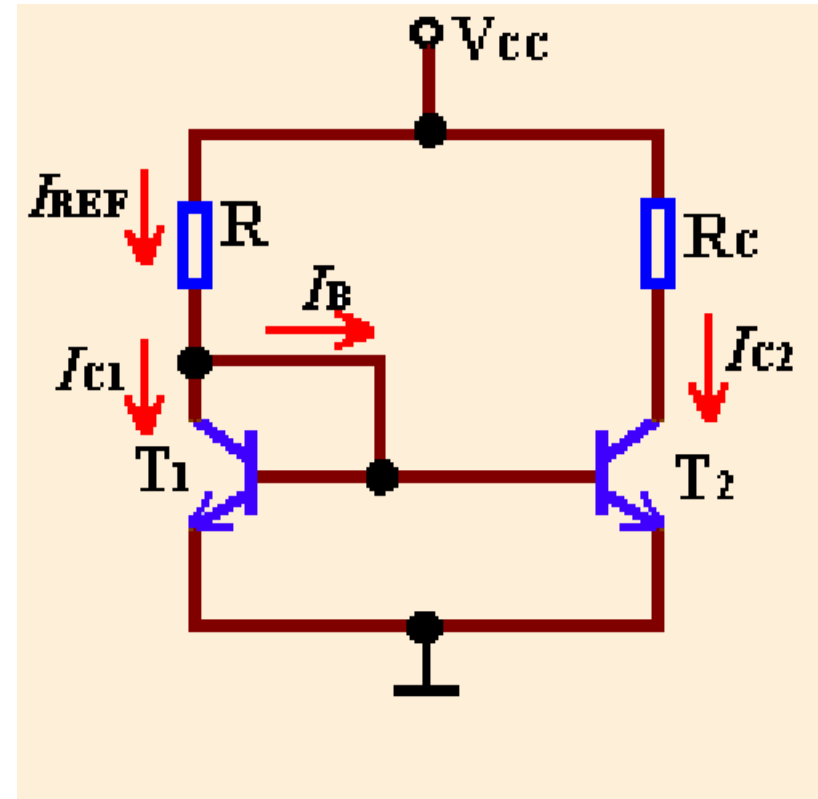

因为

$$I_c = I_s e^{\frac{V_{BE}}{V_t}} \left(1 + \frac{V_{CE}}{V_A} \right)$$

若 $V_A=100V$, $V_{CE2}=20V$

所以由基区调变效应引起的失配为


$$\frac{I_{c2}}{I_R} = \frac{1 + V_{CE2}/V_A}{1 + V_{CE1}/V_A} = \frac{1 + 20/100}{1 + 0.6/100} \approx 1.2$$

$$I_O = I_{C2} = I_{C1} = I_R - I_{B3}$$

$$I_{E3} = \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta} = \frac{2I_O}{\beta}$$

$$I_{B3} = \frac{I_{E3}}{1 + \beta} = \frac{2I_O}{\beta(1 + \beta)}$$
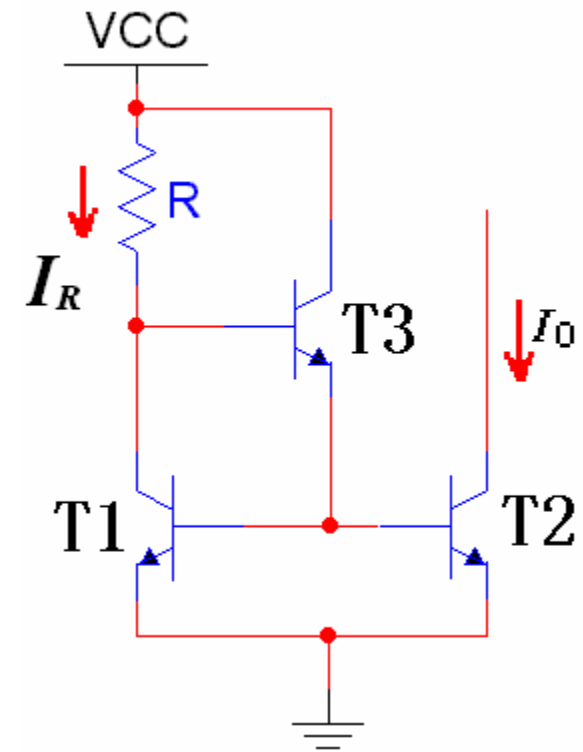
$$\therefore I_O = I_R / \left[1 + \frac{2}{\beta(1 + \beta)} \right] \approx I_R / \left(1 + \frac{2}{\beta^2} \right)$$





二. 微电流源

$$\because V_{BE1} = V_{BE2} + I_{E2}R_{e2}$$



$$I_{C2} \approx I_{E2} = \frac{V_{BE1} - V_{BE2}}{R_{e2}} = \frac{\Delta V_{BE}}{R_{e2}}$$

由于 ΔV_{BE} 很小，所以 I_{C2} 也很小。

$$\because I_C = I_S e^{V_{BE}/V_t} \quad I_{S1} = I_{S2}$$

$$\therefore V_t \ln \frac{I_{C1}}{I_{S1}} - V_t \ln \frac{I_{C2}}{I_{S2}} = I_{E2}R_{e2}$$
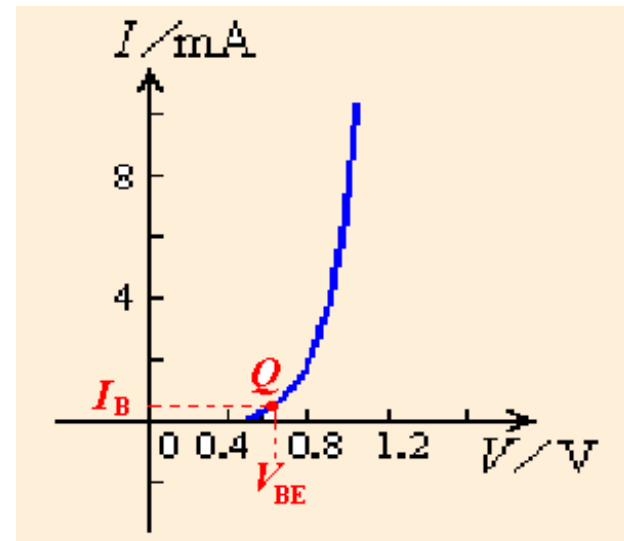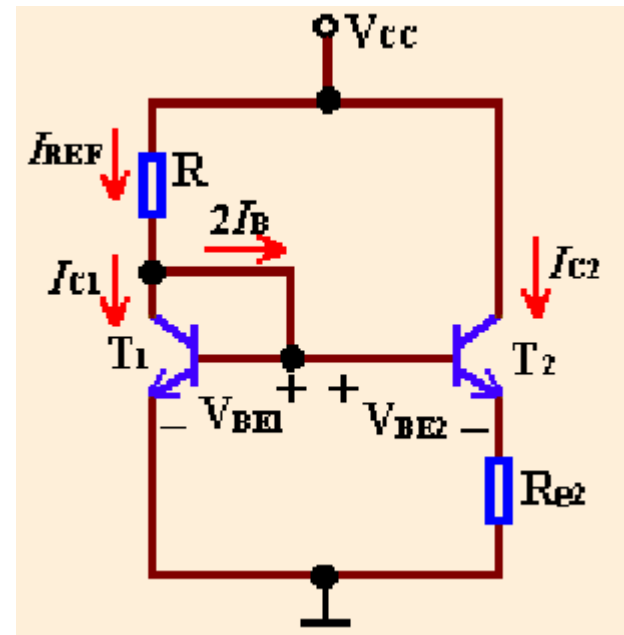
$$\therefore I_{C2}R_{e2} = V_t \ln \frac{I_{REF}}{I_{C2}}$$





三. 比例电流源





$$U_{BE1} + I_{E1}R_1 = U_{BE2} + I_{E2}R_2$$

$$U_{BE1} \approx U_{BE2}$$

$$\therefore I_{E1}R_1 \approx I_{E2}R_2$$
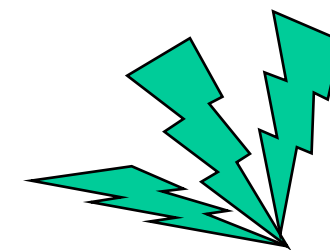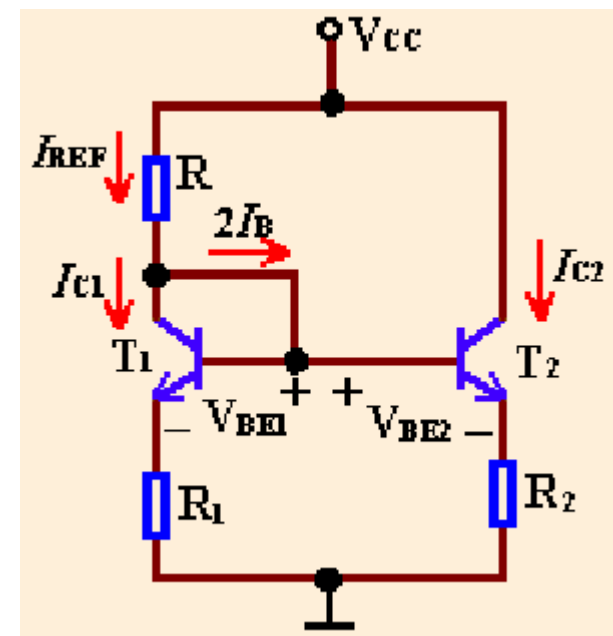
$$I_{C2} \approx \frac{R_1}{R_2} I_{C1} \approx \frac{R_1}{R_2} I_{REF}$$






四. Wilson电流源

$$I_R = I_{C1} + I_{B3} = I_{C1} + \frac{I_O}{\beta}$$

$$\left\{ \begin{aligned} I_{E3} &= I_{C2} + I_{B1} + I_{B2} = I_{C2} \left(1 + \frac{2}{\beta} \right) \\ I_{C1} &= I_{C2} \\ I_{E3} &= \frac{1 + \beta}{\beta} I_O \end{aligned} \right.$$


所以


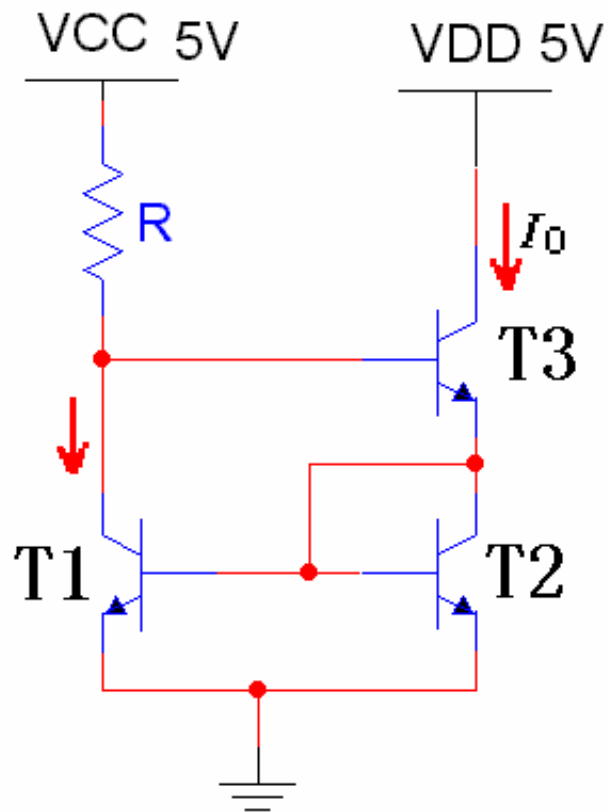
$$I_O = I_R \left(1 - \frac{2}{\beta^2 + 2\beta + 2} \right)$$







五. 多路电流源

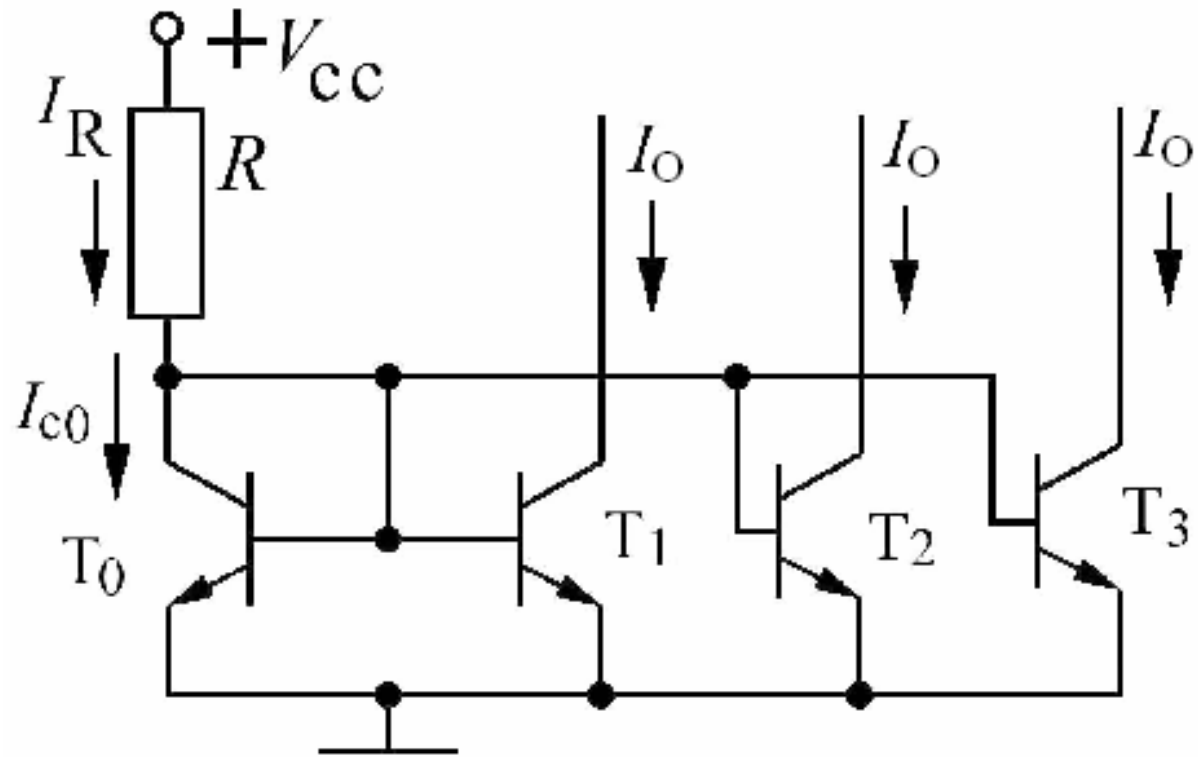

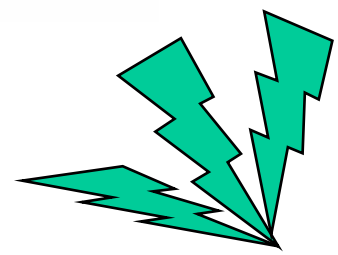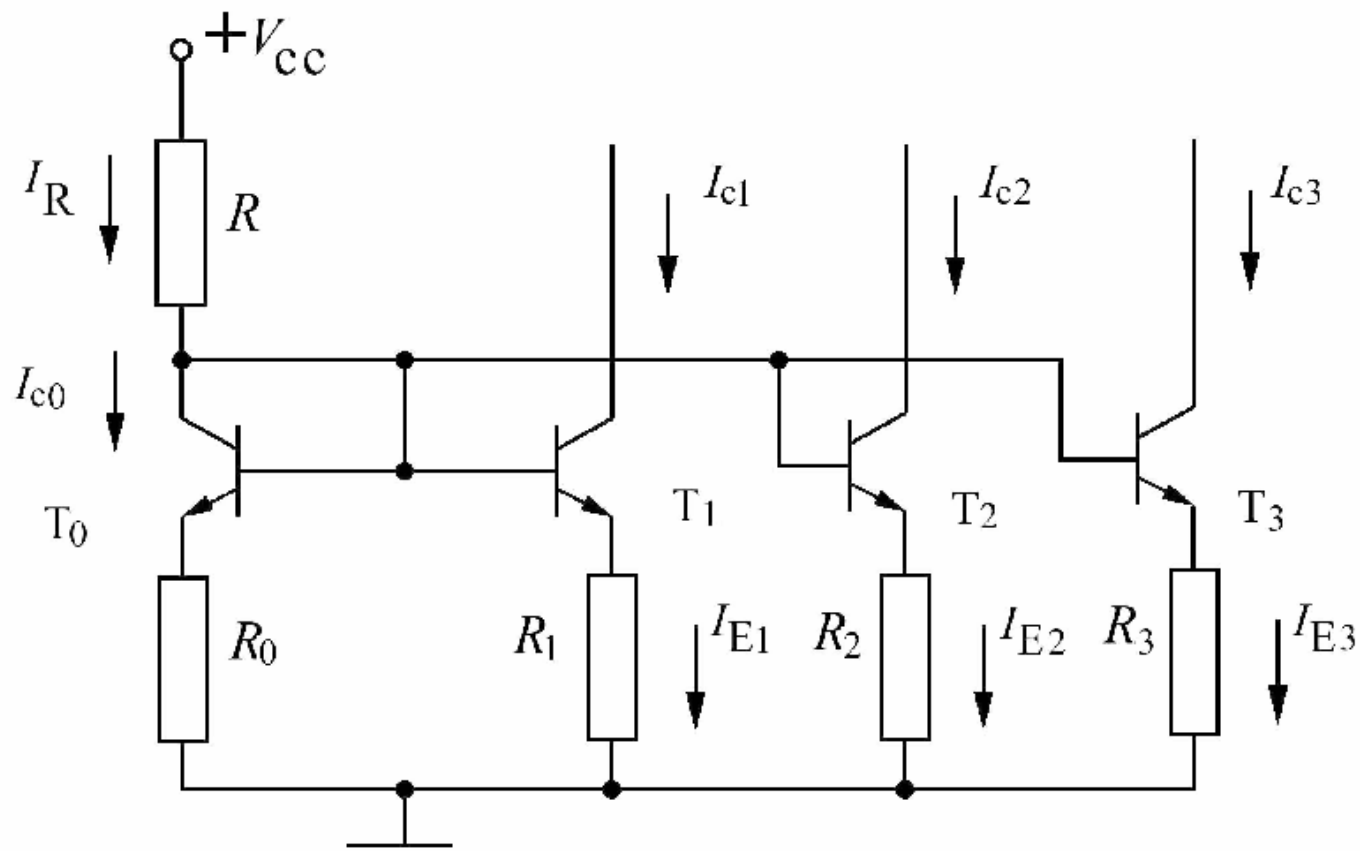

六. MOS型电流源

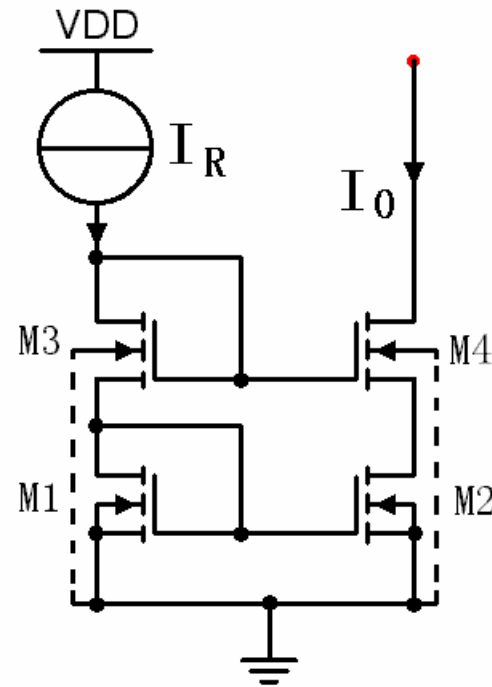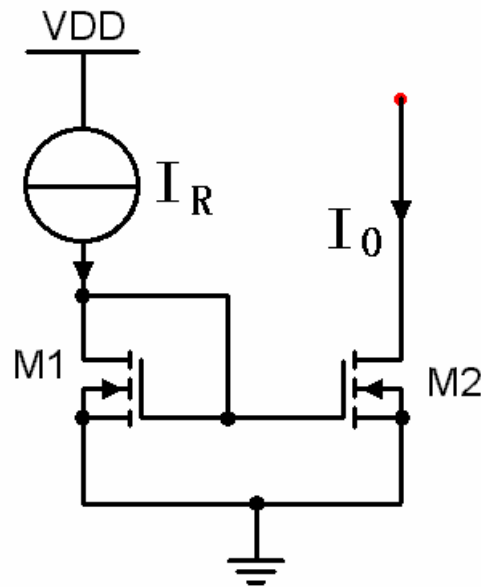

$$\frac{I_O}{I_R} = \frac{K'_2 W_2 L_1 (V_{GS2} - V_{T2})^2 (1 + |\lambda_2 V_{DS2}|)}{K'_1 W_1 L_2 (V_{GS1} - V_{T1})^2 (1 + |\lambda_1 V_{DS1}|)}$$

$$\frac{I_O}{I_R} = \frac{W_2 L_1 (1 + |\lambda_2 V_{DS2}|)}{W_1 L_2 (1 + |\lambda_1 V_{DS1}|)}$$



8.2 差动放大电路



一. 结构: 对称性结构


即: $\beta_1 = \beta_2 = \beta$

$$V_{BE1} = V_{BE2} = V_{BE}$$

$$I_{CBO1} = I_{CBO2} = I_{CBO}$$

$$r_{be1} = r_{be2} = r_{be}$$

$$R_{C1} = R_{C2} = R_C$$

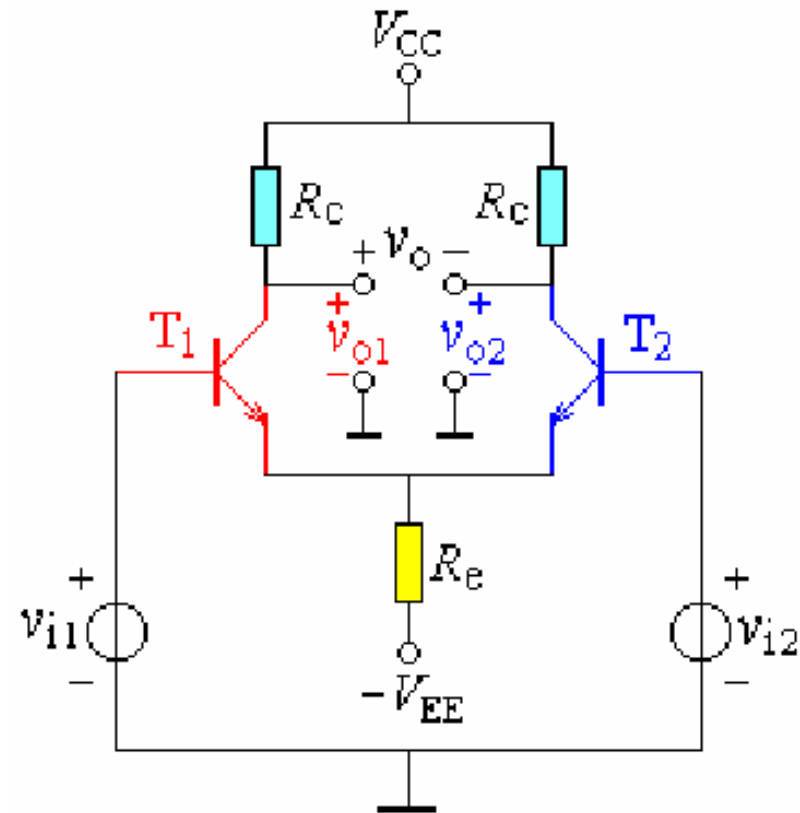

二. 几个基本概念

1. 差动放大电路一般有两个输入端:


双端输入——从两输入端同时加信号。

单端输入——仅从一个输入端对地加信号。

2. 差分放大电路可以有两个输出端，一个是集电极 C_1 ，另一个是集电极 C_2 。

双端输出——从 C_1 和 C_2 输出。

单端输出——从 C_1 或 C_2 对地输出。

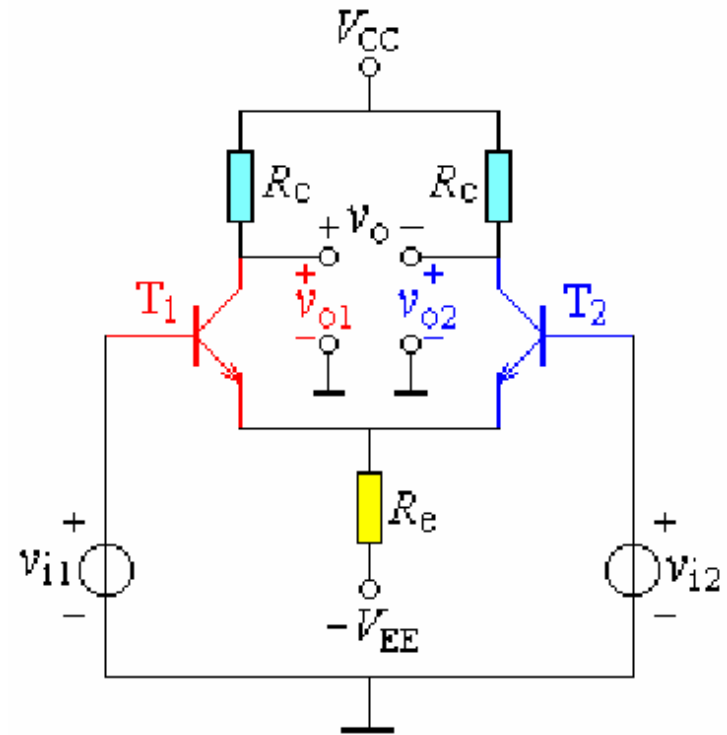

3. 差模信号与共模信号

差模信号: $v_{id} = v_{i1} - v_{i2}$

共模信号: $v_{ic} = \frac{1}{2}(v_{i1} + v_{i2})$

差模电压增益 $A_{VD} = \frac{v_{od}}{v_{id}}$


共模电压增益 $A_{VC} = \frac{v_{oc}}{v_{ic}}$

总输出电压

$$v_o = v_{od} + v_{oc} = A_{VD} v_{id} + A_{VC} v_{ic}$$

4. 共模抑制比


$$K_{CMRR} = \left| \frac{A_{VD}}{A_{VC}} \right|$$

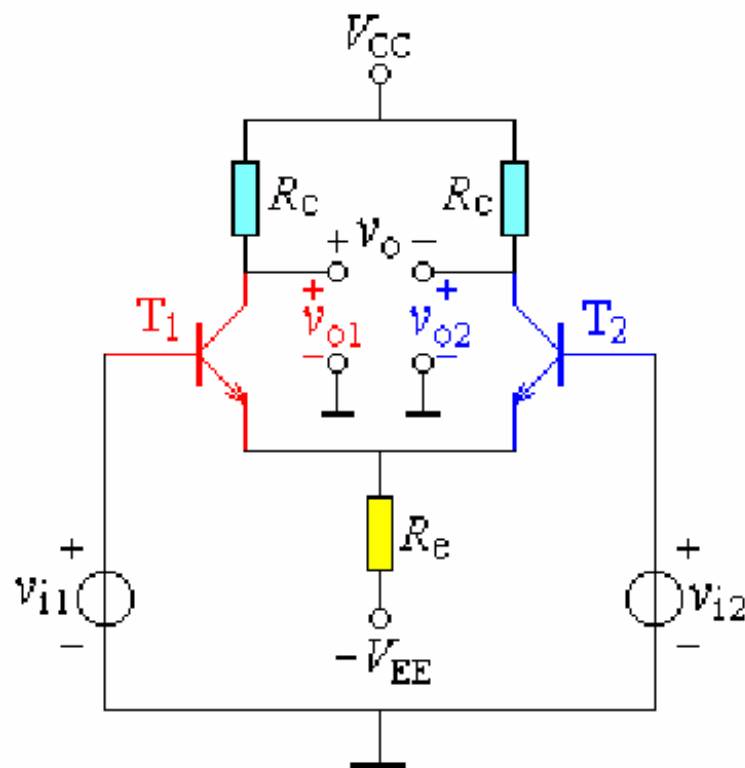

纯差模信号

大小相等，极性相反


$$u_{sd1} = -u_{sd2}$$

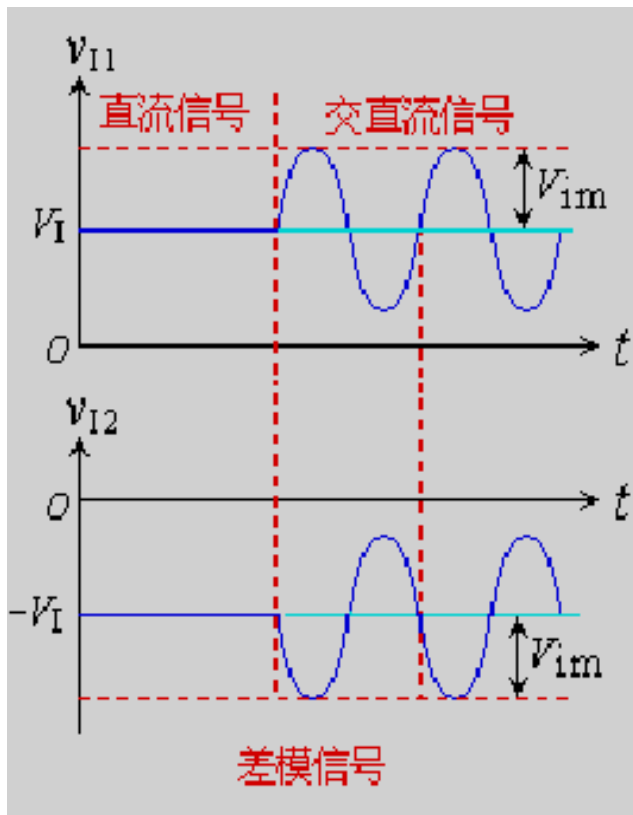

纯共模信号

大小相等，极性相同

$$u_{sc1} = u_{sc2}$$

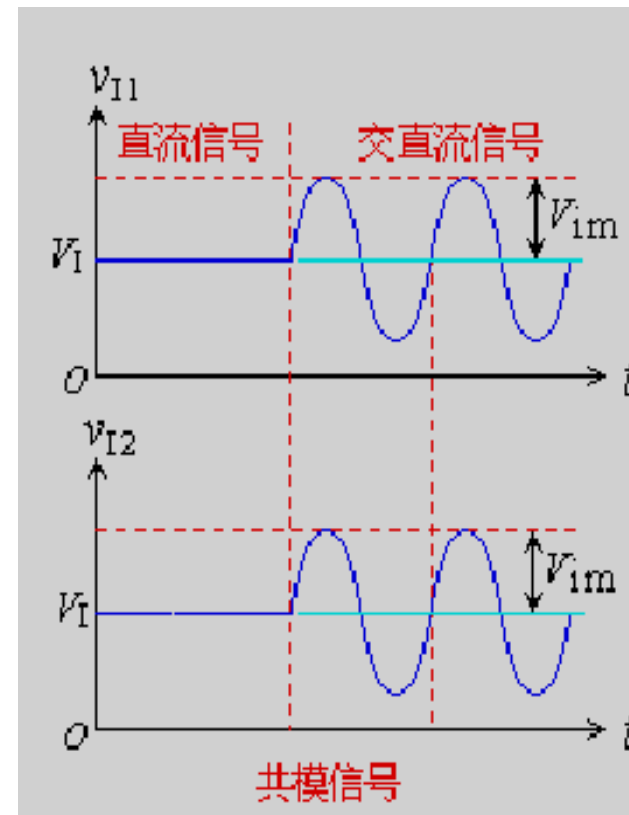


任意信号分解为共模信号和差模信号

$$\therefore \begin{cases} V_{i1} = V_{sd1} + V_{sc1} \\ V_{i2} = V_{sd2} + V_{sc2} \end{cases}$$

$$\begin{cases} V_{sd1} = -V_{sd2} \\ V_{sc1} = V_{sc2} \end{cases}$$

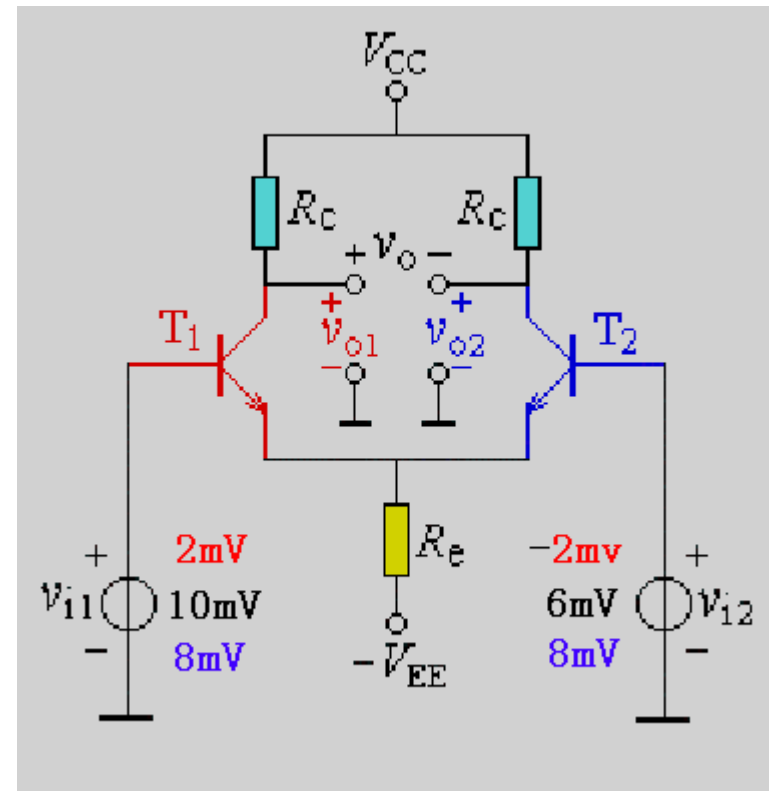
$$\therefore \begin{cases} V_{sd1} = -V_{sd2} = \frac{V_{i1} - V_{i2}}{2} \\ V_{ic1} = V_{ic2} = \frac{V_{i1} + V_{i2}}{2} \end{cases}$$




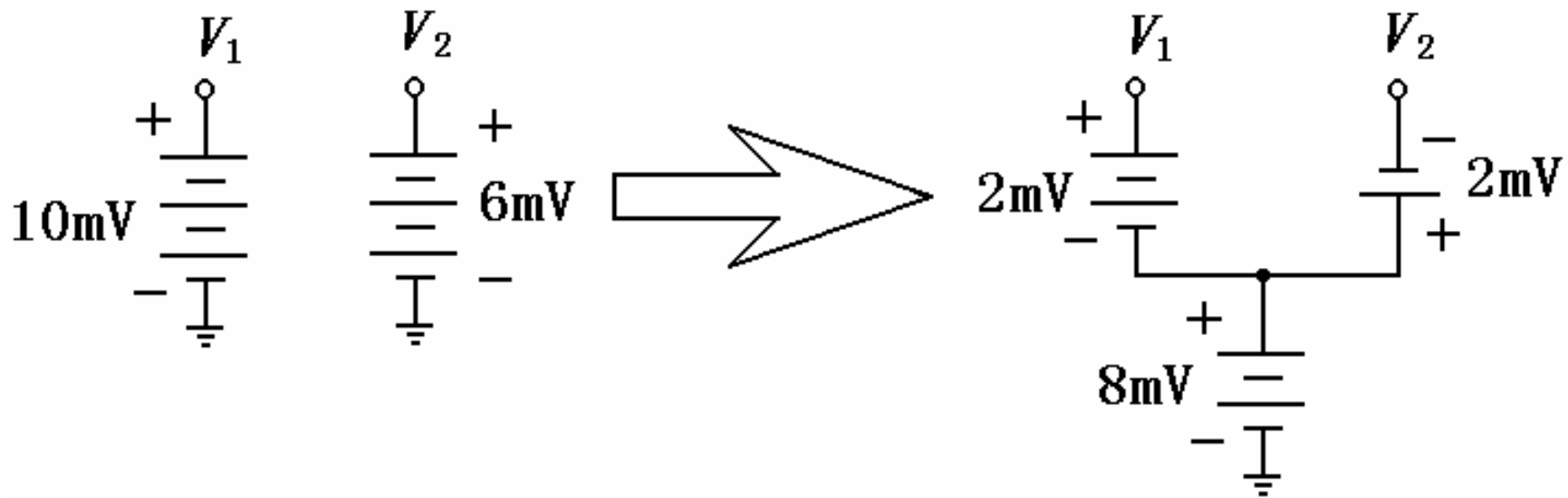例: $V_{i1}=10\text{mV}$, $V_{i2}=6\text{mV}$

$$v_{sd1} = -v_{sd2} = \frac{v_{i1} - v_{i2}}{2} = 2\text{mV}$$

$$V_{ic1} = V_{ic2} = \frac{V_{i1} + V_{i2}}{2} = 8\text{mV}$$



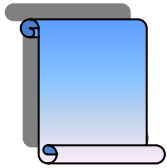

三. 差动放大电路的基本工作原理

1. 静态工作点的计算:

$$v_{i1} = v_{i2} = 0$$

忽略 I_b , 有:


$$I_{Re} = \frac{-0.7V - (-V_{EE})}{R_e}$$

$$I_{C1} = I_{C2} = I_C = \frac{1}{2} I_{Re}$$

$$\begin{aligned} V_{CE1} &= V_{CE2} \\ &= V_{CC} - I_C R_C - (-0.7) \end{aligned}$$

$$I_{B1} = I_{B2} = \frac{I_C}{\beta}$$

双端输入、双端输出

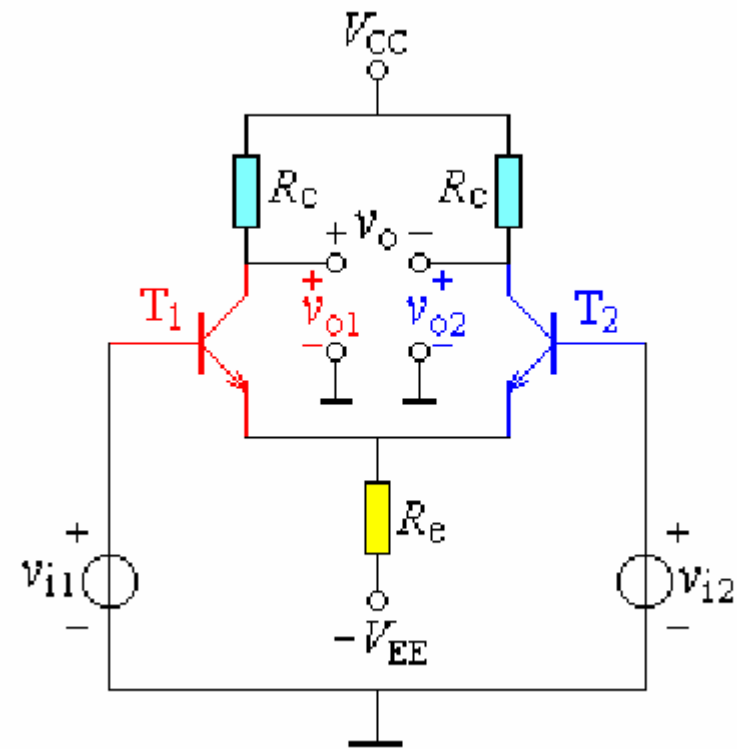

$$V_O = V_{C1} - V_{C2} = 0$$

2.抑制零漂的原理:

双端输入、双端输出

当 $v_{i1} = v_{i2} = 0$ 时,


$$v_{C1} = v_{C2}$$

$$v_o = v_{C1} - v_{C2} = 0$$

当温度变化时:

$$\Delta v_{C1} = \Delta v_{C2}$$
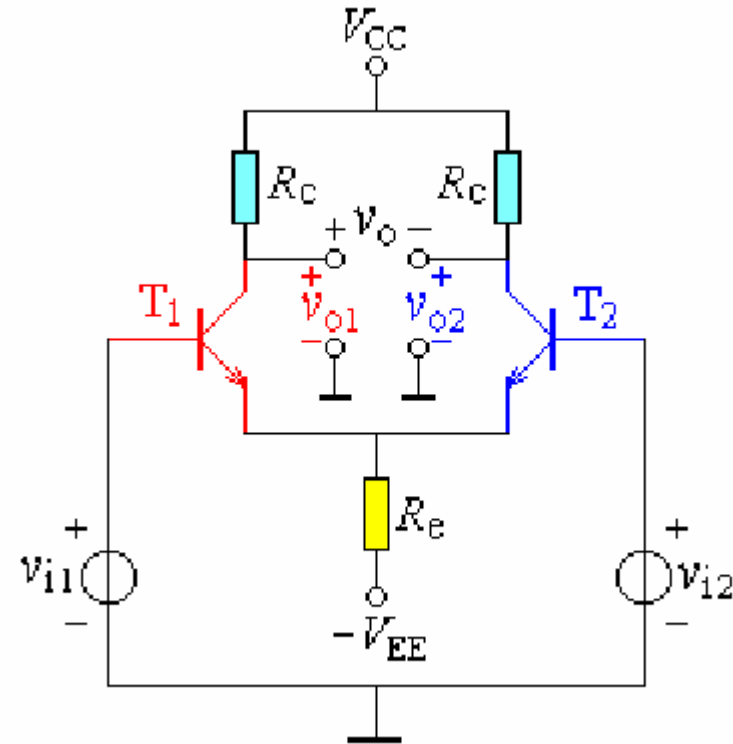
$$v_o = (v_{C1} + \Delta v_{C1}) - (v_{C2} + \Delta v_{C2}) = 0$$



3. 电路的动态分析

(1) 加入纯差模信号

设: $v_{i1} = -v_{i2} = v_{id}/2$, $v_{ic} = 0$ 。


R_e 对差模信号相当于短路

因为: 设 $v_{i1} \uparrow, v_{i2} \downarrow \rightarrow i_{b1} \uparrow, i_{b2} \downarrow$

$\rightarrow i_{e1} \uparrow, i_{e2} \downarrow \rightarrow |\Delta i_{e1}| = -|\Delta i_{e2}|$

$\rightarrow I_{Re}$ 不变 $\rightarrow V_E$ 不变

双端输入、双端输出

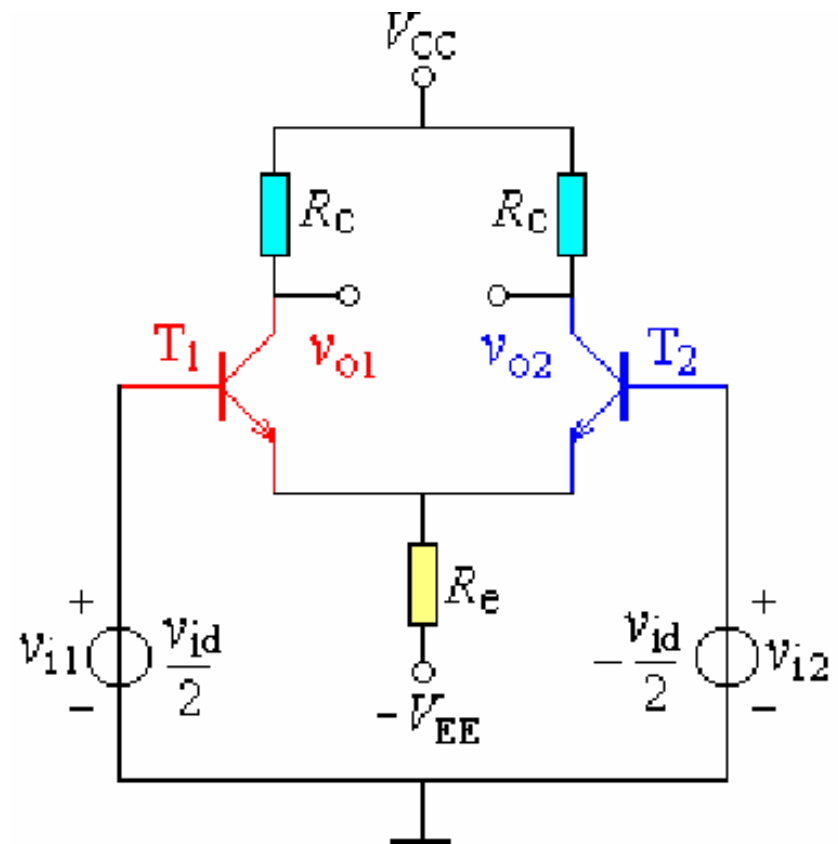

以上内容仅为本文档的试下载部分，为可阅读页数的一半内容。如要下载或阅读全文，请访问：<https://d.book118.com/21803206500006046>