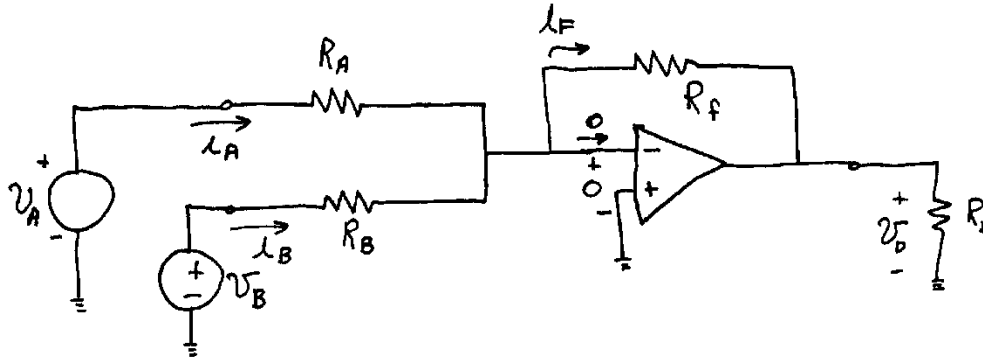


# CHAPTER 14

## Solutions for Exercises

E14.1



$$(a) \quad i_A = \frac{V_A}{R_A} \quad i_B = \frac{V_B}{R_B} \quad i_F = i_A + i_B = \frac{V_A}{R_A} + \frac{V_B}{R_B}$$


$$v_o = -R_F i_F = -R_F \left( \frac{V_A}{R_A} + \frac{V_B}{R_B} \right)$$

$$(b) \quad \text{For the } v_A \text{ source, } R_{inA} = \frac{V_A}{i_A} = R_A.$$

$$(c) \quad \text{Similarly } R_{inB} = R_B.$$

(d) In part (a) we found that the output voltage is independent of the load resistance. Therefore, the output resistance is zero.


E14.2 (a)

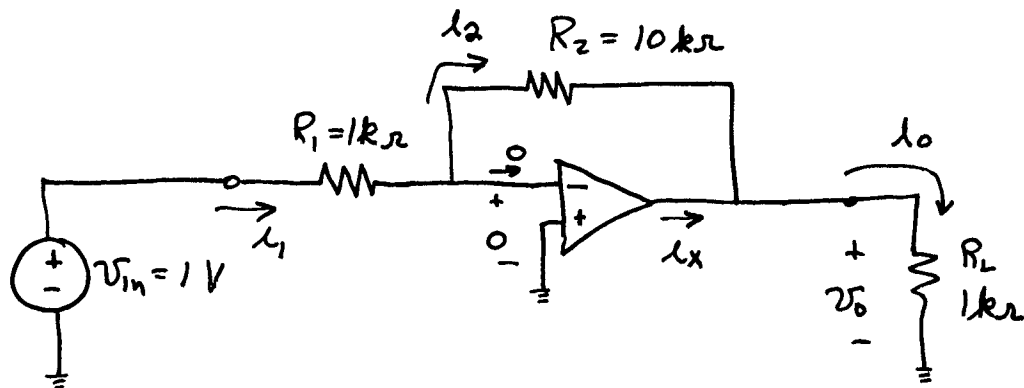

$$i_1 = \frac{V_{in}}{R_1} = 1 \text{ mA} \quad i_2 = i_1 = 1 \text{ mA} \quad v_o = -R_2 i_2 = -10 \text{ V}$$

$$i_o = \frac{v_o}{R_L} = -10 \text{ mA} \quad i_x = i_o - i_2 = -11 \text{ mA}$$


(b)

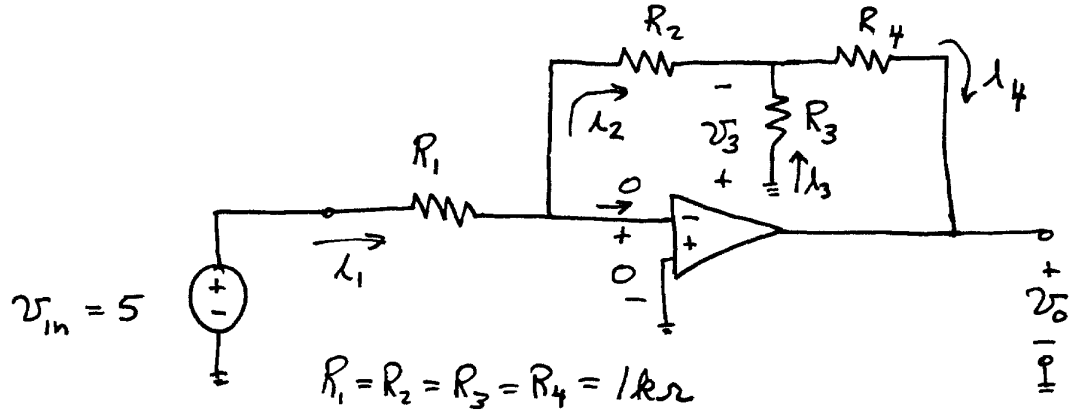

$$i_1 = \frac{v_{in}}{R_1} = 5 \text{ mA} \quad i_2 = i_1 = 5 \text{ mA} \quad v_3 = R_2 i_2 = 5 \text{ V}$$

$$i_3 = \frac{v_3}{R_3} = 5 \text{ mA} \quad i_4 = i_2 + i_3 = 10 \text{ mA} \quad v_o = -R_4 i_4 - R_2 i_2 = -15 \text{ V}$$

### E14.3

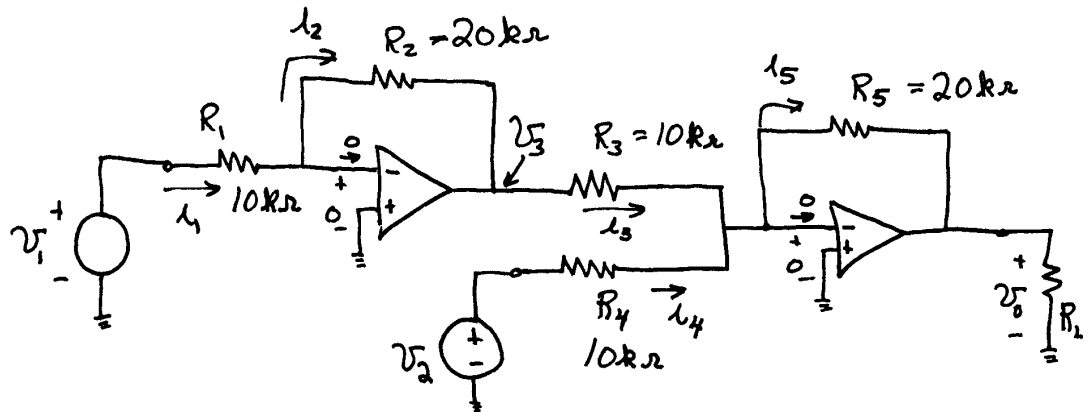


Direct application of circuit laws gives  $i_1 = \frac{v_1}{R_1}$ ,  $i_2 = i_1$ , and  $v_3 = -R_2 i_2$ .

From the previous three equations, we obtain  $v_3 = -\frac{R_2}{R_1} v_1 = -2v_1$ . Then

applying circuit laws gives  $i_3 = \frac{v_3}{R_3}$ ,  $i_4 = \frac{v_2}{R_4}$ ,  $i_5 = i_3 + i_4$ , and  $v_o = -R_5 i_5$ .

These equations yield  $v_o = -\frac{R_5}{R_3}v_3 - \frac{R_5}{R_4}v_2$ . Then substituting values and using the fact that  $v_3 = -2v_1$ , we find  $v_o = 4v_1 - 2v_2$ .

E14.4 (a)

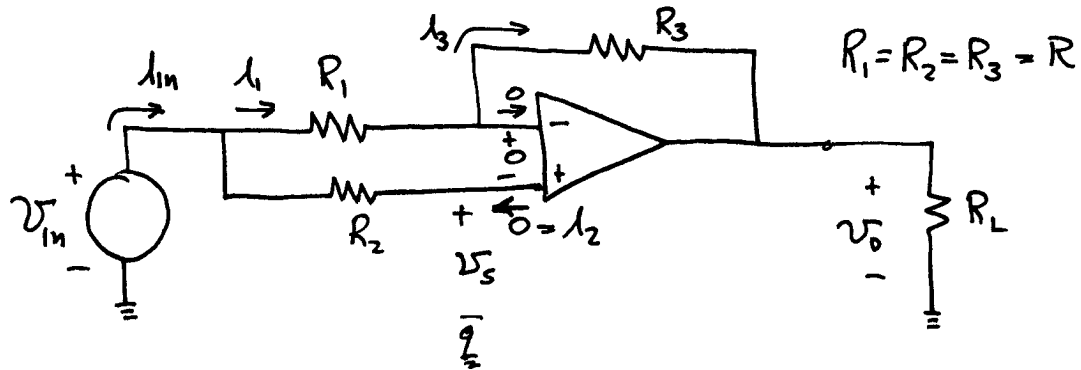


$$v_s = v_{in} + R_2 i_2 = v_{in} \quad (\text{Because of the summing-point restraint, } i_2 = 0.)$$

$$i_1 = \frac{v_{in} - v_s}{R_1} = 0 \quad (\text{Because } v_s = v_{in}.) \quad i_{in} = i_1 - i_2 = 0$$

$$i_3 = i_1 = 0 \quad v_o = R_3 i_3 + v_s = v_{in} \quad \text{Thus, } A_v = \frac{v_o}{v_{in}} = +1 \text{ and } R_{in} = \frac{v_{in}}{i_{in}} = \infty.$$

(b)

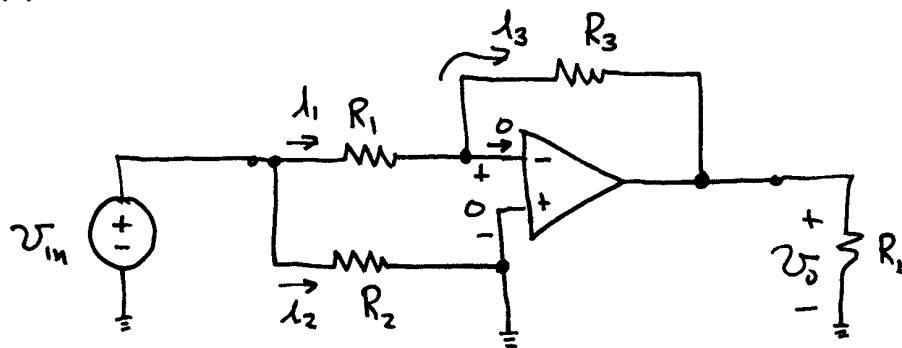


(Note: We assume that  $R_1 = R_2 = R_3$ .)

$$i_1 = \frac{v_{in}}{R_1} = \frac{v_{in}}{R} \quad i_2 = \frac{v_{in}}{R_2} = \frac{v_{in}}{R} \quad i_{in} = i_1 + i_2 = \frac{2v_{in}}{R} \quad R_{in} = \frac{R}{2}$$


$$i_3 = i_1 = \frac{v_{in}}{R_1} \quad v_o = -R_3 i_3 = -\frac{R_3}{R_1} v_{in} = -v_{in} \quad A_v = \frac{v_o}{v_{in}} = -1$$

E14.5

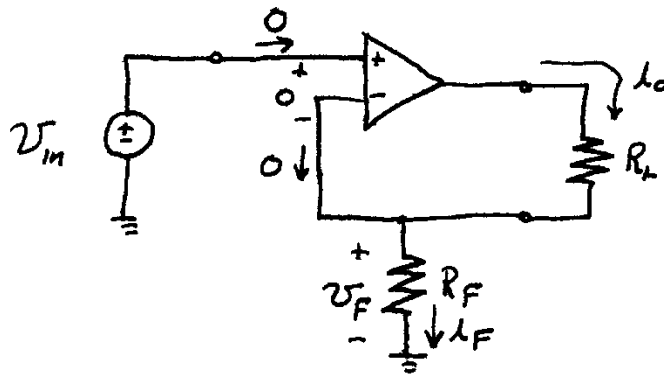

From the circuit, we can write  $v_F = v_{in}$ ,  $i_F = \frac{v_F}{R_F}$ , and  $i_o = i_F$ . From these equations, we find that  $i_o = \frac{v_{in}}{R_F}$ . Then because  $i_o$  is independent of  $R_L$ , we conclude that the output impedance of the amplifier is infinite. Also  $R_{in}$  is infinite because  $i_{in}$  is zero.

E14.6 (a)

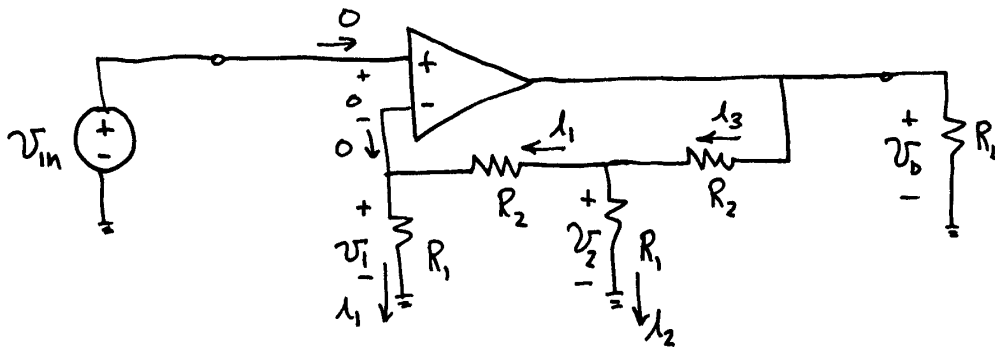

$$v_1 = v_{in} \quad i_1 = \frac{v_1}{R_1} \quad v_2 = R_2 i_1 + R_1 i_1 \quad i_2 = \frac{v_2}{R_1} \quad i_3 = i_1 + i_2 \quad v_o = R_2 i_3 + v_2$$

Using the above equations we eventually find that

$$A_v = \frac{v_o}{v_{in}} = 1 + 3 \frac{R_2}{R_1} + \left( \frac{R_2}{R_1} \right)^2$$

(b) Substituting the values given, we find  $A_v = 131$ .

(c) Because  $i_{in} = 0$ , the input resistance is infinite.

(d) Because  $v_o = A_v v_{in}$  is independent of  $R_L$ , the output resistance is zero.

以上内容仅为本文档的试下载部分，为可阅读页数的一半内容。如要下载或阅读全文，请访问：<https://d.book118.com/228071142054006026>