

Chapter 6 – Motors and Motor Control (cont'd)



#### **Outline**

- Direct current (DC) motors
  - □ Theory of operation
  - □ Control circuits
- Stepper motors
  - □ PM stepper motors
  - □ VR stepper motors
  - □ Control circuits

MECH451 + EMEB223 3



## Control circuits


- To drive the motor, an interface circuit is required to convert the low-level motor-control signal from the controller into a signal strong enough to run the motor.
- Two methods of motor speed control
  - □ Analog drive
  - □ Pulse-width modulation (PWM)

MECH451 + EMEB223 **4** 


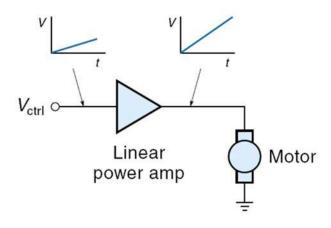
# Analog drive


- The classical way to do this is with an analog drive
  - ☐ A linear power amplifier amplifies the drive signal from the controller and gives the motor a "strengthened" analog voltage
  - □ A DAC (digital-to-analog converter) would be required if the controller is digital.



(a) Analog drive

MECH451 + EMEB223


5

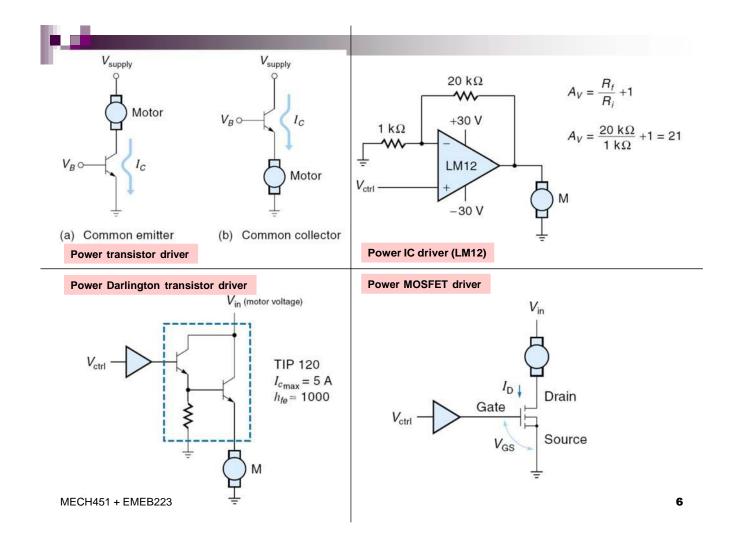


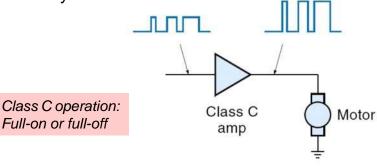
### Pulse-width modulation (PWM)

- The other technique for controlling a DC motor is **pulsewidth modulation** (PWM).
  - ☐ In this system, power is supplied to the motor in the form of DC pulses of a fixed voltage
  - ☐ The width of the pulses is varied to control the motor speed.
    - The wider the pulses, the higher the average DC voltage, so more energy is available to the motor.
  - ☐ The frequency of the pulses is high enough that the motor runs smoothly.



MECH451 + EMEB223


(b) Pulse-width modulation (PWM) drive

7


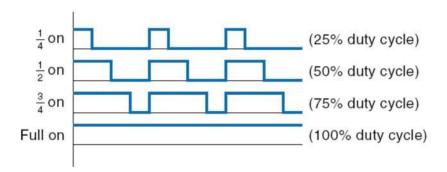
### PWM (cont'd)

- Power is supplied to the motor in a square wavelike signal of constant magnitude but varying pulse width or duty cycle.
- **Duty cycle** refers to the percentage of time the pulse is high (per cycle).



MECH451 + EMEB223 **8** 

以上内容仅为本文档的试下载部分,为可阅读页数的一半内容。如要下载或阅读全文,请访问: <a href="https://d.book118.com/41623314222">https://d.book118.com/41623314222</a> 2010040